
Contents

Chapter 1 Basic Concepts of Oscillators	1
1.1 Introduction, 1	
1.2 Summary of Network Theory, 3	
1.3 Basic Configurations of Oscillators, 12	
1.4 Oscillator Description and Specifications, 17	
1.5 Oscillator Circuit Classification, 19	
1.6 References, 20	
Chapter 2 Transistor Properties Applicable to Oscillator Design	22
2.1 Introduction, 22	
2.2 Two-Port Small-Signal Transistor Models, 22	
2.3 The Small-Signal Common Emitter Hybrid-PI Model of the Bipolar Transistor, 37	
2.4 Large-Signal Common Emitter Bipolar Transistor Characteristics, 47	
2.5 The Common Base Bipolar Transistor, 52	
2.6 Biasing of Bipolar Transistors, 57	
2.7 The Junction Field Effect Transistor, 59	
Chapter 3 Piezoelectric Resonators	66
By Arthur Ballato	
3.1 Introduction, 66	
3.2 Equivalent Circuits, 69	
3.3 Doubly Rotated Cuts, 96	
3.4 Surface Acoustic Wave (SAW) Devices, 100	
3.5 Miniature Resonators, 102	
3.6 Undesired Responses, 104	

- 3.7 Static Temperature Effects, 105
- 3.8 Aging Effects, 109
- 3.9 Environmental Effects (Excluding Static Temperature Effects), 110
- 3.10 Drive Level Effects, 114
- 3.11 Activity Dips, 118
- 3.12 Radiation Effects, 118
- 3.13 Noise in Quartz Crystals, 119
- 3.14 General Specifications, 120
- 3.15 Military Specifications, 121
- 3.16 National and International Specifications, 122

Chapter 4 Other Resonators 123

- 4.1 Inductance Capacitance Circuits (LC Resonators), 123
- 4.2 Electromechanical Resonators, 124
- 4.3 The Magnetostriction Resonator, 124

Chapter 5 The Pierce, Colpitts, Clapp Oscillator Family 125

- 5.1 Introduction, 125
- 5.2 The Idealized Oscillator, 128
- 5.3 Examples of Idealized Oscillator Applications, 130
- 5.4 Effect of the Phase Angle of g_m in the Idealized Oscillator, 136
- 5.5 The Real Oscillator, 139
- 5.6 The Theory Applied to Crystal Oscillators, 151
- 5.7 Load Impedance Transformation, 160
- 5.8 f_T and β_o Requirements, 163
- 5.9 Frequency Stability Analysis, 164

Chapter 6 Limiting 169

- 6.1 Introduction, 169
- 6.2 The Self-Limiting Single Bipolar Transistor Oscillator, Sinusoidal v_{BE} or $v_{BE'}$, 170
- 6.3 The Self-Limiting Single Bipolar Transistor Oscillator, Sinusoidal i_E , 178
- 6.4 The Self-Limiting Single Junction Field Effect Transistor Oscillator, Sinusoidal v_{GS} , 179
- 6.5 Diode Limiter, 179
- 6.6 Principal Reference, 180

Chapter 7 The Normal Pierce Oscillator 181

- 7.1 Introduction, 181
- 7.2 Oscillator Circuit Analysis, 181

7.3	Frequency Variations Due to External Factors, 192	
7.4	The Design Procedure, 194	
7.5	The Pierce Oscillator, Collector Base Limiting, 195	
7.6	The Pierce Oscillator, <i>be</i> Cutoff Limiting, 199	
7.7	Measurement Techniques for the Pierce Oscillator, 205	
Chapter 8	The Isolated Pierce Oscillator	208
8.1	Introduction, 208	
8.2	Oscillator Circuit Analysis, 208	
8.3	Limiting, 215	
8.4	The Design Procedure, 215	
8.5	Algorithm and Design Examples, 215	
Chapter 9	The Normal Colpitts Oscillator	220
9.1	Introduction, 220	
9.2	Oscillator Circuit Analysis, 221	
9.3	Frequency Variations Due to External Factors, 223	
9.4	The Design Procedure, 223	
9.5	The Colpitts Oscillator, Collector Base Limiting, 224	
9.6	The Colpitts Oscillator <i>be</i> Cutoff Limiting, 227	
Chapter 10	The Semiisolated Colpitts Oscillator	233
10.1	Introduction, 233	
10.2	Oscillator Circuit Analysis, 233	
10.3	Frequency Variations Due to External Factors, 241	
10.4	The Design Procedure, 241	
10.5	The Design Algorithm and Design Examples, 241	
Chapter 11	The Butler Oscillator	250
11.1	Introduction, 250	
11.2	Oscillator Circuit Analysis, 251	
11.3	The $X_A = 0$ Design Procedure, 264	
11.4	Theory and Design of the Stable Butler Oscillator, 268	
Chapter 12	Algorithms	280
12.1	Introduction, 280	
12.2	General Discussion of the Algorithms, 282	
	<i>Algorithm 12.1 Pierce Oscillator, Collector Limiting, 286</i>	
	<i>Algorithm 12.2 Pierce Oscillator, <i>be</i> Cutoff Limiting, 294</i>	
	<i>Algorithm 12.3 Isolated Pierce Oscillator, Collector Limiting, 302</i>	

- 13.1 Introduction, 353
- 13.2 Single Transistor Oscillators, 353
- 13.3 The Darlington Transistor Pair, 358
- 13.4 The Cascode Amplifier, 362
- 13.5 Other Oscillator Circuits, 364

- 14.1 Introduction, 369
- 14.2 General Description of the ALC Oscillator, 370
- 14.3 Description of the Components of the ALC Oscillator, 374
- 14.4 The Prediction of the Approximate Phase Noise Performance of the Oscillator, 382

- 15.1 Introduction, 383
- 15.2 Classification of Gate Elements, 384
- 15.3 Application of the Various Gate Types, 385
- 15.4 Biasing, 386
- 15.5 Conversion of Gates Having Different Functions into Equivalent Inverters, 389
- 15.6 The Inverter Approximate Equivalent Circuit, 390
- 15.7 Type of Limiting Used in Gate Oscillators, 391
- 15.8 Gate Oscillators with Crystals Operating in the Inductive Region, 392
- 15.9 Gate Oscillators with Crystals Operating Near Series Resonance, 394
- 15.10 Closing Remarks, 395

- 16.1 Introduction, 397
- 16.2 Gate Oscillators with Digital Output, 398
- 16.3 Linear Integrated Circuit Oscillators, 399
- 16.4 Miniature Packaged Crystal *Oscillators*, 400

Chapter 17	Circuitry Frequency Stability Requirements in Crystal Oscillators, Excluding the Crystal	402
17.1	Introduction, 402	
17.2	The Osci and Llator Concepts, 403	
17.3	Oscillator Relationships Using the Osci Llator Concept, 404	
17.4	Crystal Oscillators Wherein the Crystal Network Operates in the Inductive Region, 405	
17.5	Experimental Procedure for the Oscillator of Section 17.4, 406	
17.6	Crystal Oscillators Wherein the Crystal Network Operates Near Series Resonance, 407	
17.7	Experimental Determination of the Oscillating Point in the Oscillator Using the Osci and Llator Concepts, 408	
17.8	Conditions for the Applicability of Sections 17.1 to 17.7, 409	
17.9	Short-Term Performance, 409	
Chapter 18	Special Problems in Oscillators	411
18.1	Introduction, 411	
18.2	Spurious Oscillations, 411	
18.3	Spurious Signals Due to Crystal Responses, 413	
18.4	Squegging, 414	
18.5	Crystal Physical Location and Connections, 415	
18.6	Oscillator Starting, 415	
18.7	Isolation, 416	
18.8	Aging of Components 417	
18.9	<i>Oscillator</i> Testing, 417	
Chapter 19	Component and Circuitry Measurements	418
19.1	Introduction, 418	
19.2	General Characteristics of the Measurement Procedures, 419	
19.3	dc Measurements, 419	
19.4	ac Voltage and Current Measurements, 420	
19.5	The Oscilloscope as a Measurement Tool, 422	
19.6	Linear and Small-Signal Immittance Measurements, 422	
19.7	Large-Signal Immittance and Phase Measurements, 428	
19.8	Z_{LL} Measurement Procedure, 429	
	References and Bibliography	431
	List of Symbols	441
	Index	447