

---

# Index

---

- Acceleration, 110, 112, 121
  - sensitivity, 113
  - shock, 67, 110, 112, 121
  - tip-over, 110, 112
  - vibration, 92, 110, 112, 113, 119, 121
- Activity dips, crystal, 117, 118
- Aging:
  - component, 418
  - crystal, 67, 96, 100, 101, 109, 110, 119, 121
- ALC oscillator system:
  - components, description, 374–382
    - of amplifier  $K_1$ , ac, 380
    - of amplifier  $K_3$ , dc, 381
    - of comparator, 381
    - of detector,  $K_2$ , 380
  - general, 370–374
    - of  $G_M$  loop, 370–372
    - noise performance of ALC loop, 373–374
    - requirements for  $K_3$  and  $V_C$ , 372–373
  - of noise characteristics, 381–382
  - of oscillator, 374–379
  - of output amplifier, 381
  - of output filter, 382
  - $V_{REF}$ , 381
- noise:
  - performance of ALC loop, 373–374
  - phase noise, prediction of, 382
  - Pierce oscillator in, 375–377
- Algorithms, 280–352
  - for Butler oscillator, stable design, 345–352
  - for Butler oscillator,  $X_A = 0$  design, 338–344
  - conversion efficiency in, 284
  - design examples, 284. *See also* Design examples
  - form of, 282–283
  - for isolated Pierce oscillator, 301–308
  - for normal Colpitts oscillator:
    - cutoff limiting, 318–327
    - collector limiting, 309–317
  - for normal Pierce oscillator:
    - cutoff limiting, 293–300
    - collector limiting, 285–292
  - programming for, 284
  - for semi-isolated Colpitts oscillator, 328–338
  - use of, 284
- Amplifiers:
  - cascode, 362–363
  - clamped biased JFET, 63–65
  - neutralized, isolating, 416
- Amplitude-frequency, effect in crystals, 115, 117
- Angle, *see* Cuts
  - orientation, 80, 100, 106–108, 111
  - tolerance 108, 109
- Automatic level control limiting, ALC, 169–170, 369
- Bipolar transistor, 29–59
  - biasing, 57–59
  - common-base, 52–57
    - two port small signal characteristics,  $Y_{11b}$ ,  $Y_{12b}$ , and  $\alpha = h_{21b}$ , 52
  - hybrid-PI model, 53
  - large signal characteristics, 53–56
    - for sinusoidal  $i_E$ , 53–56
    - for sinusoidal  $V_{BE}$ , 53
  - common emitter, 37–51
    - large signal characteristics, 47–51
    - small signal hybrid-PI model, 37–47
    - $\beta$  calculation of, 41–43

- $f_T$ , discussion of, 42–43
- intrinsic transistor, 29, 38
- local feedback, effect upon
  - performance, 44–46
  - variation of parameters with voltage, current and temperature, 41
- $Y_{fe}$ ,  $Y_{oe}$ , and  $Y_{re}$ , calculation of, 44
- $Y_{ie}$ , calculation of, 43
- comparison of common-base and common-emitter hybrid-PI models, 54
- minimum value for  $f_T$ :
  - resonator in parallel with base and emitter, 163–164
  - resonator in series with emitter, 252
- minimum value for  $\beta_o$ , 164
- relationships for parameters, 28
- typical data:
  - for 2N918, 30–31
  - for 2N2857, 36–37
  - for 2N2947, 32–36
- Bottoming effect, 172
- Butler oscillator, 250–269
  - circuit analysis, 251–264
    - $A_{1,0}$ , gain, factor, concept of, 259
    - approximations and assumptions for, 251–252
    - design procedures, discussion of, 262–264
      - assumption A, 264
    - frequency stability relationships, 255
    - $L_o$ , calculation of, 260–261
    - limiting:
      - assumptions for, 252
      - collector base voltage limiting, 260
      - $R_{IN}$  limiting, 260
      - type of limiting used, 260
    - oscillatory conditions, derivation of, 252–255
    - $Q_{L,3}$ , calculation, effect of, 261
    - $P_A$ ,  $P_T$ ,  $P_X$ ,  $V_e$ ,  $V_L$ ,  $V_z$ , and  $Z_c$ , calculation of, 256–257
    - $R_N$ ,  $X_n$ ,  $Z_c$ , in terms of physical components, calculation of, 262
    - transistor approximations, 252
    - $Z_e$ , in terms of physical components, 255–256
  - description of, 250
  - stable Butler oscillator, theory and design of, 268–279
    - background for, 268
    - basis of design, 269
    - $C_{ce}$ , effect of, 272–273
    - design algorithm, 273, 345–352
    - design examples, 274–275, 277–278
    - oscillator relationships, 269–271
    - $Q_{op}$ , calculation of, 279
    - trimming, 276, 279
    - $X_{L,+}$  and  $X_{L,-}$ , relationships for, 271
    - $X_{A=0}$  design procedure, 257–259, 264–268
      - design algorithm, 264, 338–344
      - design example, 264–266, 267
      - $Q_{op}$ , calculation of, 261–262
      - relationships for  $X_{A=0}$ , 257–259
      - trimming, 266, 268
- $C'_L$ , calculation of, 191–192
- $C_{r2}$ , calculation of, 191, 223
- Capacitance, crystal:
  - load, 70, 71, 76, 77, 90–92, 117, 120, 121
  - motional, 70, 71, 82–85, 87–89, 91–93, 96, 97, 100, 102–104, 114, 120
  - overtone, 83, 84, 88
  - ranges, 86, 88
  - ratio, 79, 82, 85, 87, 89, 91–93, 95, 96, 100, 102, 104
  - stray, 71, 72, 76, 89, 91
  - trimmer, 77, 82
  - wiring, 76
- Capacitors, associated with crystal, 66, 74, 94
- Circuit, crystal:
  - equivalent electrical, 66, 69–71, 95, 97, 98, 101, 104, 105
  - motional arm parameters, 71, 79, 83–85, 87, 89, 91, 95, 96, 102, 104, 105
- Circuitry, oscillator, frequency stability requirements of, 402–410
- Clamp biased amplifier, 63–65
- Clamp biased limiting, 63–65, 179
- Clapp Gouriot oscillator, 167
- Clapp oscillator, *see* Pierce, Colpitts and Clapp oscillator family
- Colpitts oscillator, *see* Pierce, Colpitts and Clapp oscillator family
  - normal, 181–207
  - semi-isolated, 233–249
- Coupling in crystals:
  - mechanical, 102, 104, 105, 117
  - piezoelectric, 81, 82, 87, 89, 95, 97, 99, 109
- Crystal parameters, measurement of, 424–425
- Crystal physical location, problem due to, 415
- Crystal responses, problem due to, 413–414
- Crystal resonator, *see* Plates
- CR-numbers, 91–93
- Current, crystal,  $I_x$ , 78, 89, 114, 115, 117, 146, 151
  - measurement of, 206, 421
- Cuts, crystal, 69, 80, 82, 85, 92, 93, 100, 104, 106, 120

- doubly rotated, 96, 97, 117
  - SC, 83, 87, 88, 92, 97–100, 102, 106–108, 110–115, 117–119
- singly rotated, 97
  - AT, 81, 83, 86–89, 92, 96, 97, 99, 100, 104, 106, 107, 111–115, 117, 118
  - BT, 83, 86–88, 97, 104, 106
  - GT, 86, 87, 102, 106
  - GT, 86, 87, 102, 106
  - SL, 86, 87, 102
  - ST, 100, 117
- Darlington pair, 358–363
- Delay line, 101
- Design examples:
  - for Butler oscillator:
    - stable design, 274–276, 277–278
    - $X_A = 0$  design, 264–266, 267
  - for isolated Pierce oscillator, 216, 217–218
  - for normal Colpitts oscillator:
    - cutoff limiting, 227, 228–231
    - collector limiting, 224, 225–226
  - for normal Pierce oscillator:
    - cutoff limiting, 200, 201–204
    - collector limiting, 195, 196–198
  - for semi-isolated Colpitts oscillator, 241–248
- Design procedure, 194. *See also individual oscillator name*
- Dielectric constant, quartz, 87, 91
- Dielectric permittivity, quartz, 87, 91.
- Diode limiter, *see* Limiting, diode
- Drive level, crystal, 20, 110, 114, 115, 117–121. *See also* Activity dips; Amplitude-frequency
- Electrode, crystal, 113
  - deposition, material, 69
  - geometry, 89–91, 98, 100, 104, 105, 109, 117
  - stresses in, 98, 100, 109, 119
- Enclosures, crystal, 66, 68, 69, 90, 95, 104, 115, 120, 121
  - ambient, 69, 80, 85, 109, 110
  - geometry, 68, 104
  - material, 68
  - sealing, 68, 109, 110
  - terminals, leads, 66, 68
- Environment, crystal, 92, 110. *See also* Acceleration; Radiation; Temperature
- External limiter, 169, 364–368.
- Filter, crystal, 79, 82, 96, 101, 105, 119, 382
- Frequency:
  - characterization of, 21
  - in crystals:
    - accuracy, 67
    - antiresonance, 73, 74, 78, 79, 82, 83, 91
    - changes, 94, 96, 102, 112, 114, 117–119
    - constant,  $N_0$ , 81, 97
    - load, 71, 75, 76, 91, 93, 95, 109
    - modulation, 82, 94, 113
    - operating, 71, 74, 76, 78, 79, 82, 89, 92, 93, 96, 100, 102–104, 117, 120
    - pulling, 82, 93, 95
    - range, 67–69, 85, 95, 103
    - resonance, 73, 75, 76, 78, 82, 83, 92–95, 97, 109, 113
    - series resonance, 73, 76, 92
    - stability, 67, 83, 84, 93, 95, 97, 100, 102
    - tolerance, 92, 93, 102, 108, 109, 120
- Frequency stability, 18, 21. *See also individual oscillator circuit*
  - characterizations of, 20–21
  - circuitry, evaluation of, 402–410
  - long and short term, 18
- Frequency stability analysis:
  - in Butler oscillator, 255
  - in isolated Pierce oscillator, 193, 194, 219
  - in normal Colpitts oscillator, 192–194, 227, 232
  - in normal Pierce oscillator, 192–194, 199, 205
  - in Pierce, Colpitts and Clapp oscillator family, 164–168, 192–194
  - in semi-isolated Colpitts oscillator, 193–194, 241
- Frequency stability in LC oscillators, 123, 133
- Frequency-temperature characteristics:
  - crystal, 82, 96, 97, 100, 109, 118
  - dynamic, 110, 111
  - static, 105–107, 111
    - cubic, 99, 108, 111
    - parabolic, 108
    - turn-over, 108, 111, 112
- Gate oscillators:
  - crystal operating in inductive region, 392–393
  - crystal operating near series resonance, 394–395
  - limiting, type of, 391
- Gates:
  - biasing of, 386–388
  - classification of, 384–385
  - conversion into equivalent inverters, 389
  - inverter approximate equivalent circuit, 390–391

- Harmonic, crystal, *see* Overtone
- Holders, crystal, *see* Enclosures
  - HC-numbers, 68, 69, 81, 90, 99, 115, 122
- Hysteresis, crystal:
  - amplitude-frequency, 115
  - thermal-frequency, 112
- Immittance, 3–6
  - approximate relationships for, 4
  - polar notation, 3
  - rectangular notation, 3
  - specialized forms, 4–5
  - $Z = R + X$  representation, 5, 6
- Inductance, crystal:
  - motional, 70, 71, 83, 84, 89, 91, 97
  - overtone, 83, 84
  - region of positive, 73, 79, 83, 93, 95
- Inductors for crystals, 93–95, 102
- Integrated circuit gate oscillators, 398–399
  - Type 74124, 398
  - Type 74324, 398
  - Type 8224, 398
  - Type SP 705, 399
  - wristwatch oscillators, 399
- Integrated circuit linear oscillators, 399–400
  - Type DS 8907, 400
  - Type MC 12060, –1, and MC 12560, –1, 400
  - Type SL 680A, 400
- Inverter equivalent circuit, 390–391
- Isolated Pierce oscillator, 208–219. *See also*
  - Normal Pierce oscillator; Pierce, Colpitts and Clapp oscillator family
- advantages of, 208
  - circuit analysis, 208–215
    - additional design equations, 211–214
    - basic equations, 208–211
    - practical values of  $R_s$ , 214
    - $R_L$ , for minimum power consumption, calculation of, 214–215
  - design procedure, 215
  - design algorithm, 215, 301–308
  - design examples, 216, 217–218
  - trimming, 216, 219
  - frequency stability, 219
  - limiting, 215
- Isolation, 18, 208, 234, 235, 282, 416–417
- Junction field effect transistors (JFET), 59–65. *See also* Transistors
  - clamp biased amplifier circuit, 63–65
  - common source large signal characteristics, 62–65
  - ideal small signal characteristics, 59–61
  - noise properties, 59, 379
  - small signal high frequency characteristics, 61–62
- Leeson oscillator noise model, 382
- Limiting:
  - ALC, 169–170, 369
  - diode, 179–180, 365, 366
  - external, 169, 364–368
  - self:
    - bipolar transistor, sinusoidal  $i_E$ , 178–179
      - advantages of, 178–179
      - collector base voltage, 179
      - $R_{IN}$ , 179
    - bipolar transistor, sinusoidal  $v_{BE}$ , 170–178
      - advantages of, 170–171
      - base emitter cutoff, 171–172
      - collector base voltage, 172–178
        - when  $R_E = 0$ , 175–176
        - when  $R_E \gg r_{e0}$ , 176–178
    - JFET, sinusoidal,  $v_{GS}$ , 179
      - clamp biased, 179
      - drain gate voltage, 179
- Linear two port networks, 7–12, 22–28
  - parameters for, 7–12, 22–28
    - conversion:
      - between h and y, 24
      - between h and z, 25
      - between s and y, 25
      - between y and z, 12
    - definition:
      - of h, y, z, 7–9
      - of s, 24
    - relationships for, 9–10
  - Y networks, relationships for, 10–11
- Lithium niobate, 68
- Lithium tantalate, 68, 104
- Llator, 79, 92
  - concept, 14, 403–404
  - measurement of, 423–424, 429–430
- Load impedance transformation, 160–163
  - capacitance coupling network, 162
  - capacitive divider coupling network, 161
  - PI coupling network, 162
  - transformer coupling network, 161
- Local oscillator, 130–131
  - narrow range, 130–131
  - wide range, 130
- Losses, circuit components, 261, 283
  - ambient, 80, 85
  - crystal, *see* Mount; Trapping
  - internal friction, 80
  - mounting, 80, 81, 85

- Measurements:
- ac current, 206, 421
  - ac voltage, 420–421
  - dc current, 420
  - dc resistance, 420
  - dc voltage, 419
  - large signal immittance, 428–430
    - three terminal networks, 428–429
      - $Z_{LL}$ , 429–430
  - oscilloscope, with, 422
  - $Q_{op}$ , 206–207
  - small signal impedance, 422–428
    - c mode selector, 424
    - crystal parameters, 424–425
    - linear and non-linear components, 423, 424, 425–428
    - overtone selector, 424
    - passive components, 423
    - transistors, 425–428
      - $Z_{LL}$ , 423–424
- Merit, figure of, crystal, 74, 81, 82, 90, 92, 93, 95, 100, 102, 104
- Miller effects, 149–150, 235–237, 262–263, 272–273, 363
- Miller oscillator, 133
- Miniature packaged crystal oscillators, 400–401
- Mode selection networks, 155–160, 240
  - measurement of, 424
- Modes of vibration, 69, 80, 82–84, 117
  - a, b, c thickness, 69, 97, 107
  - separation, 97, 98
  - spectrum, 96, 98, 99, 105, 113
  - unwanted, 84, 104, 105, 121
- Motion, crystal
  - distribution of, 89–91, 98, 104
  - at edges, 81
  - measure of,  $\Psi$ , 89, 91, 98
- Motional arm, *see* Circuit, crystal
- Mount, crystal
  - bonding, 69, 109
  - losses, 80, 85, 89
  - stresses, 109, 110
  - support structure 69, 85, 104, 121
- Noise:
  - circuit components, 381
  - crystal, 110, 119
    - amplitude-to-frequency, 120
    - equivalent resistance, 119
    - flicker, higher-order, 119
    - polarization, 114
    - voltage, 119
  - oscillator, 375–377. *See also* ALC oscillator system
    - oscillator spectrum of, 375–377, 382
    - phase prediction of, 382
    - transistor, 379
- Non-linear two port networks, 12
- Normal Colpitts oscillator, 220–232. *See also* Normal Pierce oscillator; Pierce, Colpitts and Clapp oscillator family
  - circuit analysis, 221–223
    - $C_{r2}$ , calculation of, 223
    - $R_L$  and  $V_L$ , calculation of, 221–222
    - $V_E$ , calculation of, 223
  - description of, 220
  - design procedure, 223–232
    - be cutoff limiting, 227–232
      - design algorithm, 227, 318–316
      - design examples, 227, 228–231
      - trimming, 227, 232
    - collector base voltage limiting, 223–227
      - design algorithm, 224, 309–317
      - design examples, 224, 225–226
      - trimming, 224, 227
  - frequency stability, 192–194, 227, 232
- Normal Pierce oscillator, 181–207. *See also* Pierce, Colpitts and Clapp oscillator family
  - amplitude variation due to changes in  $V_{BB}$ , 193–194
  - $C'_L$ , calculation of, 191–192
  - $C_{r2}$ , calculation of, 191
  - circuit analysis, 181–192
    - fundamental design equations, 185–186
      - $g_m$ , calculation of, 190–191
    - modified PCCF equations, 182–184
    - $R_L$  and  $V_{Lmax}$ , calculation of, 186–189
    - $V_E$ , calculation of, 189–190
  - description of, 181
  - design procedure, 194–205
    - be cutoff limiting, 199–205
      - design algorithm, 199, 293–300
      - design examples, 200, 201–204
      - trimming, 200, 205
    - collector base voltage limiting, 194–199
      - design algorithm, 195, 285–292
      - design examples, 195, 196–198
      - trimming, 198
  - frequency variations due to external factors, 192–194, 199, 205
    - changes in load  $R_L$ , 192–193
    - changes in  $V_{BB}$ , 193, 194
  - measurement techniques
    - $I_3$  or  $I_x$ , 206
    - $Q_{op}$ , 206–207

## Osci:

- concept, 14, 402, 403
- replacement for inductive crystal, 405
- replacement for series resonant crystal, 407

## Oscillator:

- circuit:
  - names of, 3
  - selection, 280–281
- classification of, 2
  - abbreviations for, 2
- crystal, other circuit configurations, 353–368
  - Colpitts, low harmonic and noise, 356
  - Darlington pair Colpitts, 361–362
  - high-efficiency, 357
  - low frequency, 354–356
  - two transistor, 364–368
    - diode limiting, 365, 366
    - emitter coupled, 365, 367–368
    - and limiter, 364–365
    - semi-isolated Colpitts with cascode, output circuit, 363
    - with separate variable gain control, 365, 367
- definition of, 1, 17
- delay line, 101
- harmonic, definition of, 2
- models for, 13–17
  - feedback, 15–17
  - negative conductance/resistance, 13–15
- names of, 3
- problems, 411–417
  - aging of components, 418
  - crystal physical location, 415
  - isolation, 416–417
  - spurious oscillations, 411–413
  - spurious signals due to crystal responses, 413–414
- squegging, 414–415
- starting, 415–516
  - hysteresis, 415–416
- starting, 415–416
- temperature compensated crystal, TCXO, 82, 109
- turn-on, turn-off, 109
- variable crystal (VCXO), 82, 93

## Oscillator:

- definition of, 17
- vs. oscillator, 18
- specifications, 18
- test of, 417

## Oven, 92, 112

- noise performance, effect on, 119
- reference point, 112

time constant, 111

turn-on, turn-off, 109–111

## Overtone, crystal:

- high, 83, 95
- number, 69, 80, 82–85, 97–100, 104, 114, 117, 120
- units, 80, 86, 91

## Overtone selection networks, 153–155, 157–160, 240

measurement of, 424

Phase angle of  $g_m$ , effect of, 137–138

## Phase noise:

- curves of, 376–377
- prediction of, 382

## Pierce, Colpitts and Clapp oscillator family, 125–180

idealized oscillator, 128–138

crystal oscillator, 133–136

crystal inductive region, 133–136

crystal in series resonance or capacitive region, 95, 136

LC oscillator examples, 130–133

phase angles of  $g_m$ , effect of, 136–138

## real oscillator, 139, 160

assumptions and conditions, 141–142

circuit design equations, derivation of, 145–151

$C_{bc}$  contribution of, 149–150

currents and voltages, 146–149

oscillator operating Q, calculation of, 150

power, output, 146

$X_2$ , 147–148

## crystal oscillator, 151–160

fundamental wide frequency, range oscillators, 152–155

mode selection circuits, 155–160

overtone selection circuits, 153–155

## frequency stability analysis, 164–168

crystal oscillators, in, 167–168

stabilizing capacitor  $C'_L$ , 165–167

## oscillatory equations, calculation of, 142–145

amplitude equation, 144

frequency equation, 145

negative resistance, 144

Pierce oscillator, *see* ALC oscillator system;

Isolated Pierce oscillator; Normal

Pierce oscillator; Pierce, Colpitts

and Clapp oscillator family

Plates, crystal, *see* Electrode, crystal

dimensions, 81, 90, 91, 103

geometry:

- bevelled, contoured, 81, 91, 98, 105, 117
- flat, 69, 80–82, 84, 87, 88, 98, 104, 117
- Polarization, crystal, 113, 114, 120
- Pole-zero spacing, crystal, 79, 82, 90, 95, 97, 100
- Power level, crystal, 20, 78, 115, 118
- $Q_{op}$ , 79–80, 150–151. *See also specific oscillator circuit listed by name*
  - measurement of, 206–207
- Quality factor, crystal,  $Q_x$ , 78–81, 89, 92, 93, 95, 96, 100–104, 118, 119
- Quartz, 68, 104
  - cultured, natural, 68, 118
  - etching of, 115, 119
  - impure, swept, 68, 118, 119
  - surface preparation, 108, 115
- Quartz cuts, *see* Cuts
- Radiation, 118, 119
- Reactance, crystal:
  - change with frequency, 75, 78
  - equivalent series, 72, 73, 76, 83, 93
  - motional, 77
  - positive, 79
  - sharpness, 79
  - slope, 76, 78, 79, 84, 92–95
  - variable, varactor, 94
  - zeros, 73, 83
- Realizable maximum values:
  - of resistance of resistor, 6–7, 214
  - of resistance of tuned load, 6
- Required value of  $\beta_o$ , 164
- Required value of  $f_T$ :
  - sinusoidal  $i_E$ , 252
  - sinusoidal  $v_{BE}$ , 163–164
- Resistance, crystal, 100–104, 114, 115, 117, 119
  - apparent, 114, 118
  - change, with temperature, 80, 102
  - equivalent series, 72, 73, 76, 78, 83, 90, 102
  - load, 71, 75, 77, 80, 90, 92, 120, 121
  - motional, 70, 71, 73, 83, 84, 88–93, 96, 97
  - overtone, 84, 87
  - ranges, 87
  - shunt, 95, 96, 114, 120
- Resonance-antiresonance spacing, crystal, 79, 82, 90, 95, 97, 100
- Resonance curve, crystal:
  - sharpness, 79
  - width, 79
- Resonators, crystal, 66, 70, 122
  - bulk, BAW, 67, 100, 101, 117
  - ceramic, 68, 95, 96
  - miniature, 84, 92, 102, 104
  - one-, two-port, 70, 71, 101, 102
  - other
    - electromechanical, 124
    - inductance capacitance (LC), 123
    - magnetostriction, 124
    - surface, SAW, 67, 92, 100–102, 117
- Responses, crystal modal, *see* Modes of vibration
- Selection:
  - mode, 155–160, 240
  - oscillator circuit, 280–281
  - overtone, 153–155, 240
- Self-limiting, *see* Limiting, self
- Semi-isolated Colpitts oscillator, 233–249. *See also* Colpitts oscillator; Normal Colpitts; Pierce, Colpitts and Clapp oscillator family
  - circuit analysis, 233–240
  - description of, 233
  - isolation characteristics, 234, 235
  - limiting, 237
  - Miller effects, 235–237
  - overtone and mode selection, 240
  - $R_L$ , calculation of, 238
  - $R_{2ac}$ , calculation of, 239–240
  - $V_E$  and  $V_{Lmax}$ , calculation of, 238
  - design procedure, 241
  - design algorithm, 241
  - design examples, 241–248
  - trimming, 248–249
  - frequency variation due to external factors, 241
- Specifications:
  - crystal, 94, 115, 120–122
  - oscillator, 18–19
- Spurious oscillations, 411–413
- Spurious signals due to crystal responses, 413–414
- Squegging, 414–415
- Stability, frequency, *see* Frequency, stability
- Stabilizing capacitor,  $C'_L$ , 165–167
- Stable Butler oscillator, *see* Butler oscillator
- Stable LC oscillator, 132–133
- Stiffness, crystal, 76, 82, 100
- Stress compensation, crystal, 98, 99
- Temperature, crystal:
  - compensation, 82, 94
  - frequency stability over, 92, 100, 108
  - inflection, 100, 107, 108
  - operating range, 67, 80, 92, 93, 100, 102, 108, 109, 112, 118, 120, 121

- reference, 105, 108, 111, 120
- transients, 98, 100, 110, 111, 118, 119
- Temperature coefficients, crystal:
  - first order, 96, 98, 99, 103–105, 107, 117
  - higher order, 103–108
- Time constant:
  - crystal, motional, 80, 85, 87, 89, 90, 97, 99
  - oven, 111
- Transistors, 22–46. *See also* Bipolar transistors; Junction field effect transistors
  - comparison of JFET and bipolar transistor properties, 60
  - Darlington connection, two port small signal parameters:
    - conversion among common base/gate, common collector/drain and common emitter/source parameters, 26–28
    - conversion among  $h$ ,  $s$ ,  $y$ ,  $z$  parameters, 12, 24–25
    - notation for, 23–24
- Trapping, energy, 90, 104
- Trimming:
  - for Butler oscillator:
    - stable design, 276, 279
    - $X_A = 0$  design, 266, 268
  - for isolated Pierce oscillator, 216, 219
  - for semi-isolated Colpitts oscillator, 248–249
  - for normal Colpitts oscillator:
    - collector cutoff limiting, 224, 227
    - cutoff limiting, 227, 232
  - for normal Pierce oscillator:
    - collector limiting, 198–199
    - cutoff limiting, 200, 205
- Vibration, crystal, *see* Acceleration; Modes of vibration
  - coupled, 69, 103
  - edge, 103
  - extension, 69, 103
  - flexure, 69, 102, 103, 117
  - shear, 69, 102, 103
  - types of, 69, 80, 82, 84, 85, 102, 103
- Voltage, crystal, 113–115
- Wristwatch oscillators, 399
- $Y$  admittance, 3–4
- $Y$  networks, 9–12
- $Y$  parameters, 7–8
- $Z$  impedance, 3–4
- $Z = R + X$ , representation, 5–6
- $Z$  networks, 10
- $Z$  parameters, 8